


Course No: EQUP 2307
Course Title: Electric Circuits 1
Date: 14/01/2018
No. of Questions: (6)
Time: 2 hours
Using Calculator (Yes)

University of Palestine

Final Exam
1st. 2018-2017
Total Grade: 50


Instructor Name: Eng. M. Timraz
Student No.: _____
Student Name: _____
College Name: _____
Dep. / Specialist: _____
Using Dictionary (No)

Question One:

(05/50)


- A) What is the total capacitance in the circuit?
What is the charge on the plate of the $6\mu\text{f}$ capacitor?

2.5 Pt.

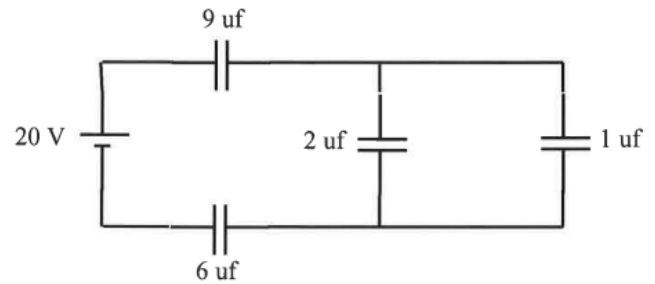

- B) Calculate what value of R_L will absorb maximum power and find the maximum power for the circuit in the following Figure.

2.5 Pt.

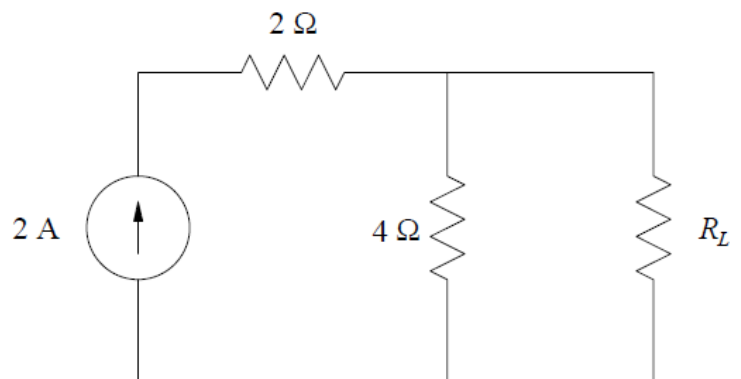

Course No: EQUIP 2307
 Course Title: Electric Circuits 1
 Date: 14/01/2018
 No. of Questions: (6)
 Time: 2 hours
 Using Calculator (Yes)

University of Palestine

 Final Exam
 1st. 2018-2017
 Total Grade: 50


Instructor Name: Eng. M. Timraz
 Student No.: _____
 Student Name: _____
 College Name: _____
 Dep. / Specialist: _____
 Using Dictionary (No)

Question Two:

(05/50)

Find the equivalent resistance R_{ab} in the circuit in the following figure.
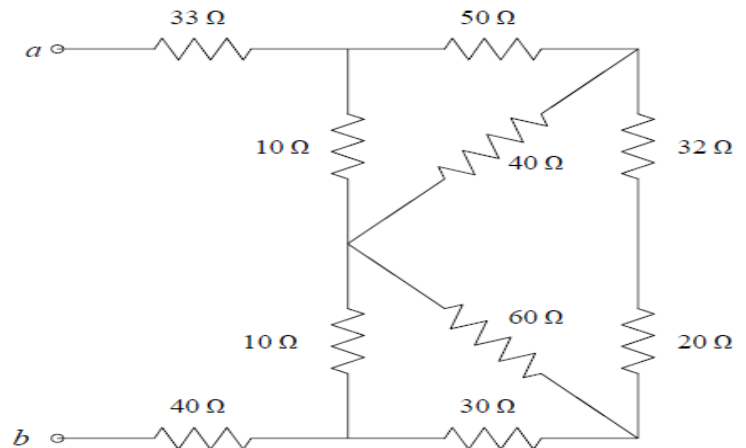
$$\begin{aligned} R_a &= \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1} & R_1 &= \frac{R_b R_c}{R_a + R_b + R_c} \\ R_b &= \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2} & R_2 &= \frac{R_c R_a}{R_a + R_b + R_c} \\ R_c &= \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3} & R_3 &= \frac{R_a R_b}{R_a + R_b + R_c} \end{aligned}$$



Course No: EQUP 2307
Course Title: Electric Circuits 1
Date: 14/01/2018
No. of Questions: (6)
Time: 2hours
Using Calculator (Yes)

University of Palestine


Final Exam
1st. 2018-2017
Total Grade: 50

Instructor Name: Eng. M. Timraz
Student No.: _____
Student Name: _____
College Name: _____
Dep. / Specialist: _____
Using Dictionary (No)

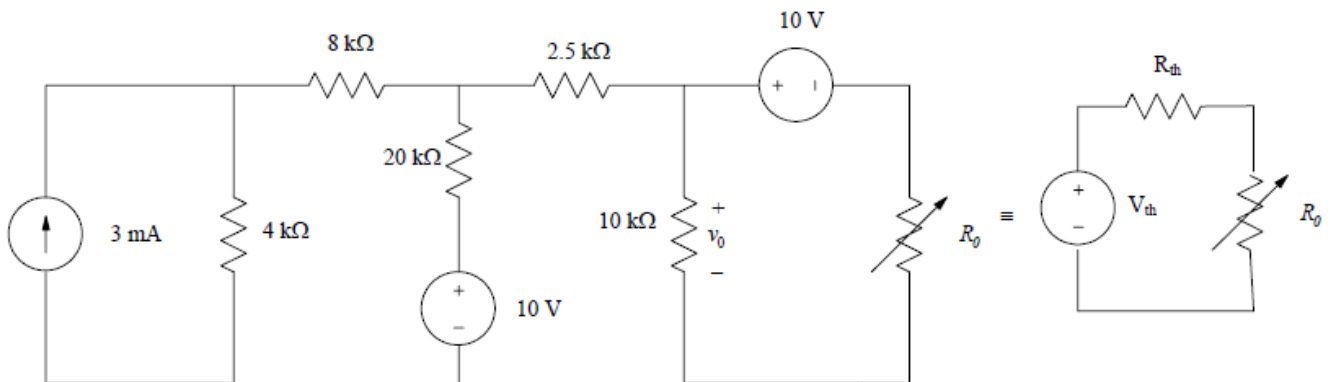Question Three: (10/50)

The variable resistor in the following circuit is adjusted for maximum power transfer to R_0 .

- Find the value of R_0 .
- Find the maximum power that can be delivered to R_0 .



Course No: EQUP 2307
Course Title: Electric Circuits 1
Date: 14/01/2018
No. of Questions: (6)
Time: 2 hours
Using Calculator (Yes)

University of Palestine


Final Exam
1st. 2018-2017
Total Grade: 50

Instructor Name: Eng. M. Timraz
Student No.: _____
Student Name: _____
College Name: _____
Dep. / Specialist: _____
Using Dictionary (No)

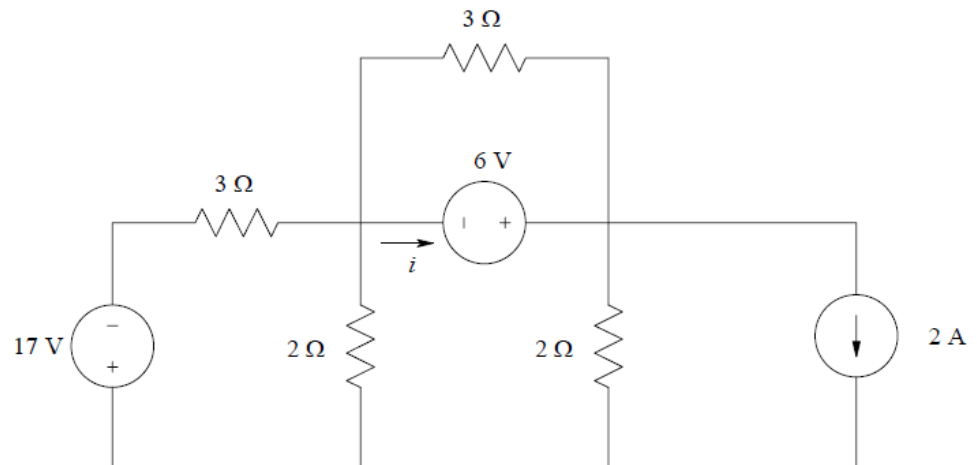Question Four:

(10/50)

Use the principle of superposition to find i in the circuit in the Figure below.



Course No: EQUP 2307
Course Title: Electric Circuits 1
Date: 14/01/2018
No. of Questions: (6)
Time: 2 hours
Using Calculator (Yes)

University of Palestine


Final Exam
1st. 2018-2017
Total Grade: 50

Instructor Name: Eng. M. Timraz
Student No.: _____
Student Name: _____
College Name: _____
Dep. / Specialist: _____
Using Dictionary (No)

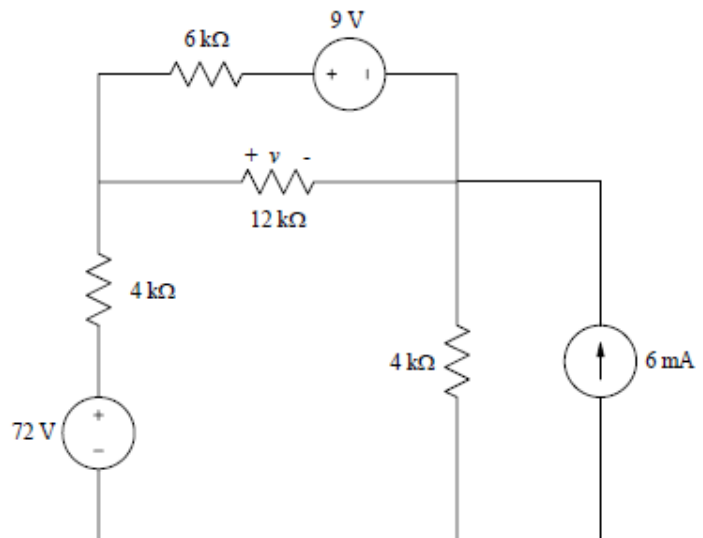Question Five:

(10/50)

Find V in the circuit in figure below by using source transformation.



Course No: EQUP 2307
Course Title: Electric Circuits 1
Date: 14/01/2018
No. of Questions: (6)
Time: 2 hours
Using Calculator (Yes)

University of Palestine


Final Exam
1st. 2018-2017
Total Grade: 50

Instructor Name: Eng. M. Timraz
Student No.: _____
Student Name: _____
College Name: _____
Dep. / Specialist: _____
Using Dictionary (No)

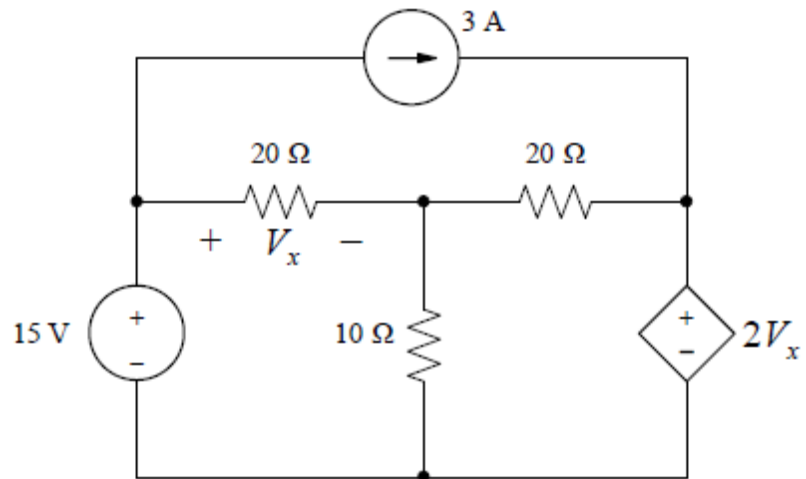Question Six:

(10/50)

In the circuit below, find the voltage V_x using mesh analysis.



End of Questions
Good Luck