

Course No: EQUP 2302
Course Title: Electric Circuits II.
Date: 11 / 03 / 2017
No. of Questions: ____3____
Time: 60 min.
Using Calculator (Yes)

University of Palestine




1st Midterm Exam
2nd Term 2016/2017
Total Grade: 20

Instructor Name: Eng. M. Timraz
Student No.: _____
Student Name: _____
College Name: Engineering
Dep. / Specialist: Biomedical Eng.
Using Dictionary (No)

Q1) Find I_o in the circuit below:

(05/15)

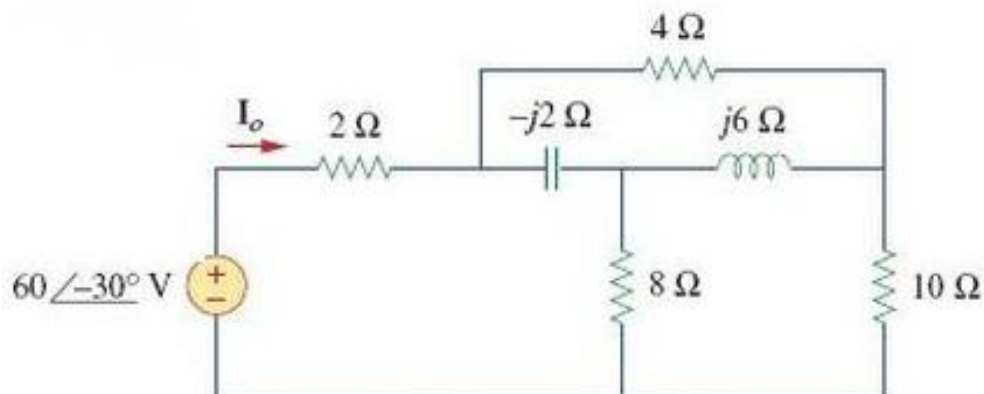

Course No: EQUP 2302
Course Title: Electric Circuits II.
Date: 11 / 03 / 2017
No. of Questions: ____3____
Time: 60 min.
Using Calculator (Yes)

University of Palestine



1st Midterm Exam
2nd Term 2016/2017
Total Grade: 20

Instructor Name: Eng. M. Timraz
Student No.: _____
Student Name: _____
College Name: Engineering
Dep. / Specialist: Biomedical Eng.
Using Dictionary (No)

Q2) If an $R = 0.5\text{-k}\Omega$ resistor, is connected in series with a combined parallel capacitor $C = 5\text{-}\mu\text{F}$, and an $L = 2\text{-mH}$ inductor with a $V(t) = 50 \sin (200t)$ volts source, what is the maximum current delivered by the source? Draw the circuit (05/15)

Course No: EQUP 2302
Course Title: Electric Circuits II.
Date: 11 / 03 / 2017
No. of Questions: ____3____
Time: 60 min.
Using Calculator (Yes)


University of Palestine



1st Midterm Exam
2nd Term 2016/2017
Total Grade: 20

Instructor Name: Eng. M. Timraz
Student No.: _____
Student Name: _____
College Name: Engineering
Dep. / Specialist: Biomedical Eng.
Using Dictionary (No)

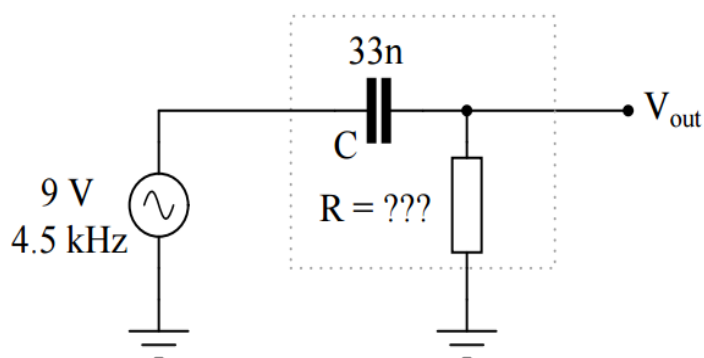Q3) Determine the necessary resistor value to give the output voltage a phase shift of 58° ? (5/15)



Good Luck.