

Course No: SWEN 2301  
Course Title: Electronics Principles  
Date: 11/01/2018  
No. of Questions: (3)  
Time: 2 hours  
Using Calculator (No)

University of Palestine  
  
Final Exam  
1<sup>st</sup>. 2018-2017  
Total Grade: 50

Instructor Name: Eng. M. Timraz  
Student No.: \_\_\_\_\_  
Student Name: \_\_\_\_\_  
College Name: \_\_\_\_\_  
Dep. / Specialist: \_\_\_\_\_  
Using Dictionary (No)

**Question One:**

**(10/50)**

Chose the correct answer, then put it in the following table

1	2	3	4	5	6	7	8	9	10

- Three different Q points are shown on a dc load line. The upper Q point represents the:
  - minimum current gain
  - intermediate current gain
  - maximum current gain
  - cutoff point
- A transistor has a  $\beta_{DC}$  of 250 and a base current,  $I_B$ , of 20  $\mu$  A. The collector current,  $I_C$ , equals:
  - 500  $\mu$  A
  - 5 mA
  - 50 mA
  - 5 A
- When transistors are used in digital circuits they usually operate in the:
  - active region
  - breakdown region
  - saturation and cutoff regions
  - linear region
- Voltage-divider bias provides:
  - an unstable Q point
  - a stable Q point
  - a Q point that easily varies with changes in the transistor's current gain
  - a Q point that is stable and easily varies with changes in the transistor's current gain
- A current ratio of  $I_C/I_E$  is usually less than one and is called:
  - beta
  - theta
  - alpha
  - omega

Course No: SWEN 2301  
Course Title: Electronics Principles  
Date: 11/01/2018  
No. of Questions: (3)  
Time: 2 hours  
Using Calculator (No)

University of Palestine




Final Exam  
1<sup>st</sup>. 2018-2017  
Total Grade: 50

Instructor Name: Eng. M. Timraz  
Student No.: \_\_\_\_\_  
Student Name: \_\_\_\_\_  
College Name: \_\_\_\_\_  
Dep. / Specialist: \_\_\_\_\_  
Using Dictionary (No)

- 
6. With the positive probe on an NPN base, an ohmmeter reading between the other transistor terminals should be:
    - a) open
    - b) infinite
    - c) low resistance
    - d) high resistance
  7. In a Common-Emitter configuration, an emitter resistor is used for:
    - a) stabilization
    - b) ac signal bypass
    - c) collector bias
    - d) higher gain
  8. To operate properly, a transistor's base-emitter junction must be forward biased with reverse bias applied to which junction?
    - a) collector-emitter
    - b) base-collector
    - c) base-emitter
    - d) collector-base
  9. The ends of a load line drawn on a family of curves determine:
    - a) saturation and cutoff
    - b) the operating point
    - c) the power curve
    - d) the amplification factor
  10. What is the current gain for a common-base configuration where  $I_E = 4.2 \text{ mA}$  and  $I_C = 4.0 \text{ mA}$ ?
    - a) 16.80
    - b) 1.05
    - c) 0.20
    - d) 0.95

Course No: SWEN 2301  
Course Title: Electronics Principles  
Date: 11/01/2018  
No. of Questions: (3)  
Time: 2 hours  
Using Calculator (No)


University of Palestine  
  
Final Exam  
1<sup>st</sup>. 2018-2017  
Total Grade: 50

Instructor Name: Eng. M. Timraz  
Student No.: \_\_\_\_\_  
Student Name: \_\_\_\_\_  
College Name: \_\_\_\_\_  
Dep. / Specialist: \_\_\_\_\_  
Using Dictionary (No)

**Question Two: (10/50)**

*Which of the following statements is true or false?  
Please put  $\surd$  or  $\times$  below the question's number in the following table*


1	2	3	4	5	6	7	8	9	10

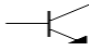1. A decrease in base current of a C-E amplifier causes the voltage measured between the emitter and the collector to increase.
2. The voltage measured from the collector to the emitter is the sum of the voltage base-emitter plus the voltage collector-base.
3. This is a PNP transistor. 
4. A transistor used in a digital circuit will have two operating states, which are cutoff and saturation.
5. In a BJT, the collector current is approximately equal to the base current.
6. The voltage gain of a transistor is inversely proportional to the change in output current.
7. When troubleshooting a bipolar junction transistor using an ohmmeter, if one of the junctions reads low in both directions, the junction is shorted and the transistor is bad. If one of the junctions reads high in both directions, the junction is shorted and the transistor is good.
8. A common-emitter (C-E) is so called because the emitter is connected to both the input and output signals.
9. With a common-collector (C-C) amplifier the input is applied to the base and the output is taken from the emitter.
10. VCE approximately equals Vcc when a transistor switch is cut off.

**Question Three: (10/50)**

A) Consider the common emitter amplifier given in the following circuit;

**5 Pt.**

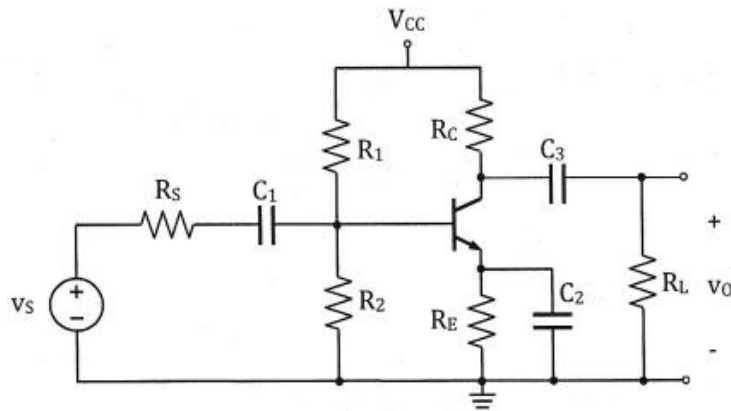

Circuit Parameters

- $V_{CC} = 12\text{ V}$
- $R_1 = 100\text{ K}$
- $R_2 = 15\text{ K}$
- $R_E = 1\text{ K}$
- $R_C = 4\text{ K}$
- $R_S = 1\text{ K}$
- $R_L = 12\text{ K}$


Transistor Parameters

- $\beta = 100$
- $V_{BE(ON)} = 0.7\text{ V}$
- $V_A = \infty$

Under DC conditions, determine the voltage gain.

B) If  $V_{CC} = +18\text{ V}$ , voltage,  $R_1$  is  $4.7\text{ k}\Omega$ , and  $R_2$  is  $1500\Omega$ .  
 What is the base bias voltage?  
 What are the collector and emitter currents?

**5 Pt.**

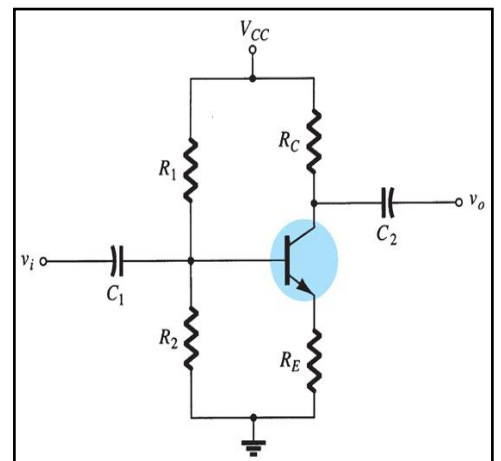



**Question Four:**


**(05/50)**

A) Determine  $R_o$  to set  $I_{c1} = I_{c2} = 2\text{mA}$ ?

**5 Pt.**

Let  $V_1 = V_2 = 0$  in the DC analysis.

Where  $I_E = I_{E1} + I_{E2}$

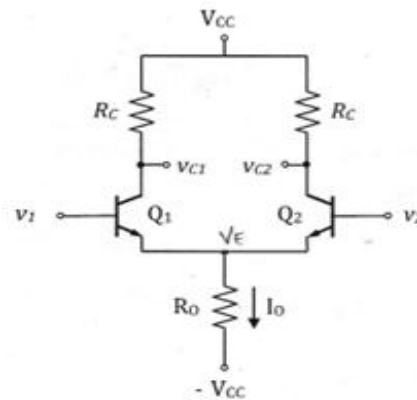

*Circuit Parameters*


$V_{CC} = 12\text{ V}$   
 $R_C = 3\text{ k}\Omega$

*Transistors' Parameters*

$V_{T1} = 27\text{ mV}$   
 $V_{T2} = 25\text{ mV}$   
 $\beta = 100$   
 $V_{BE(on)} = 0.7\text{ V}$   
 $V_A = \infty$

B) Determine the maximum voltage for the output shown circuit and PIV for each Si diode?

**5 Pt.**

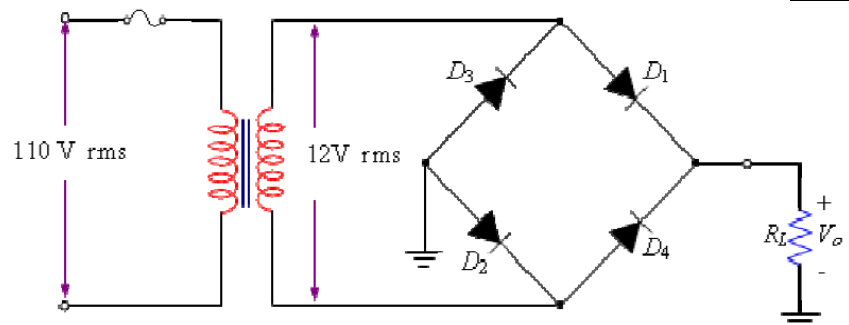

Course No: SWEN 2301  
 Course Title: Electronics Principles  
 Date: 11/01/2018  
 No. of Questions: (3)  
 Time: 2 hours  
 Using Calculator (No)

University of Palestine  
  
 Final Exam  
 1<sup>st</sup>. 2018-2017  
 Total Grade: 50

Instructor Name: Eng. M. Timraz  
 Student No.: \_\_\_\_\_  
 Student Name: \_\_\_\_\_  
 College Name: \_\_\_\_\_  
 Dep. / Specialist: \_\_\_\_\_  
 Using Dictionary (No)


**Question Five:** **(05/50)**

A) For the following amplifier circuit:

2.5 Pt.

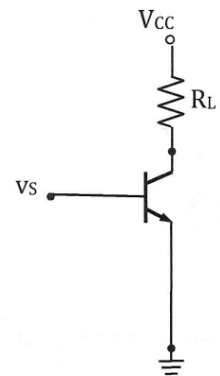- a) Draw the DC load line and determine the class of power amplifier.
- b) Determine  $I_{CQ}$  assuming the  $Q$  point is at the center of the DC load line.


Where  $V_{CC} = 15\text{ V}$ ,  $R_L = 15$  and  $V_{CE(SAT)} = 0\text{V}$ .



B) Determine the currents  $I_1$ ,  $I_2$ , and  $I_{D2}$  for the network of the following figure.










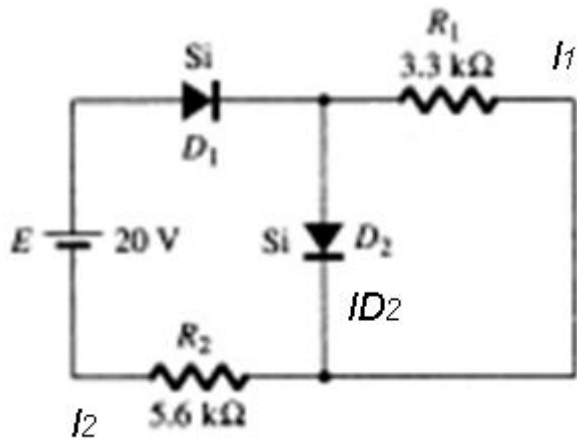
2.5 Pt.

Where  $R_1 = 3.3\text{ k}\Omega$ ,  $R_2 = 5.6\text{ k}\Omega$ .



**Question Six: (5/50)**

Draw the output signal for each figure below.

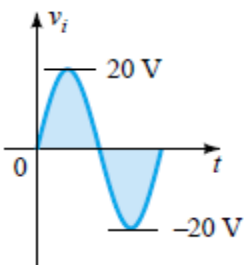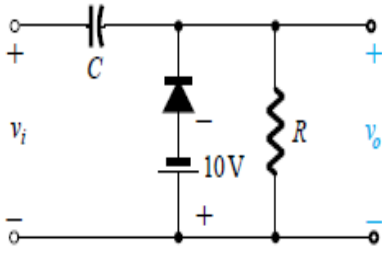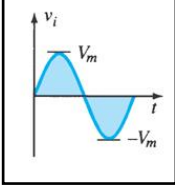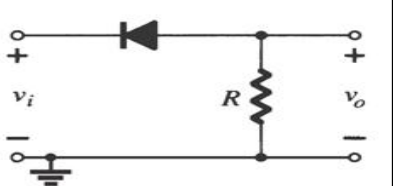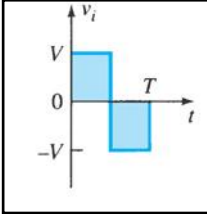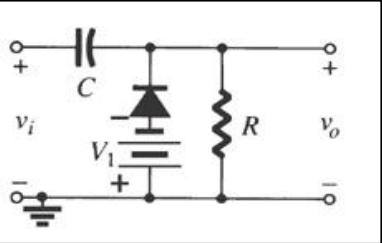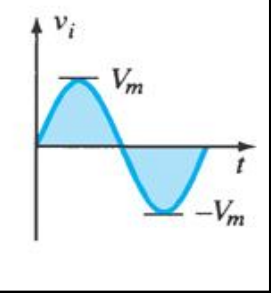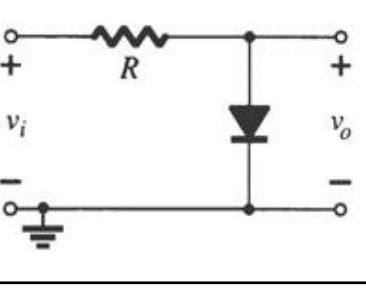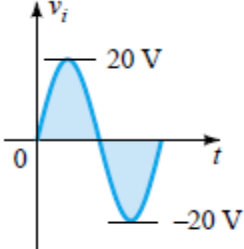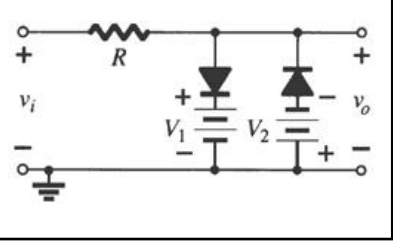No.	Input	Circuit	Output
1.			
			
			
4.			
5.			

End of Questions  
 Good Luck