

Course No: SWEN2301
Course Title: Electronics Principles
Date: 26/11/2018
No. of Questions: (4)
Time: 1 hours
Using Calculator (Yes)

University of Palestine

Second Midterm Exam
2018-2019
Total Grade:30

Instructor Name: Dr. Alaa AbuZaiter
Student No.: _____
Student Name: _____
College Name: Engineering
Dep. / Specialist: Software Eng.
Using Dictionary (No)

Question One:

8 Marks

A) Defined the followings: (4 Marks)

a) **p-n Junction:**

b) **Diode Array:**

c) **Clamper:**

d) **Inductor:**


B) What are the differences between **Half Wave Rectifier** and **Full Wave Rectifier**?
(4 Marks)

Half Wave Rectifier	Full Wave Rectifier



Question Two:

(8 Marks)

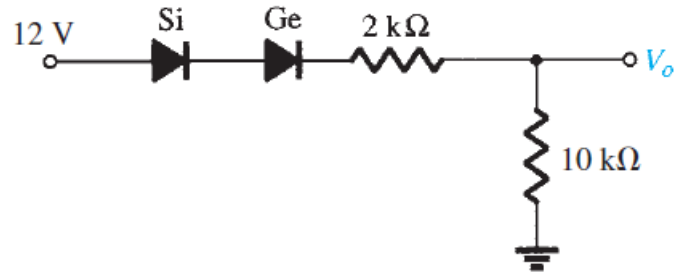
1. Find V_o , I_{R1} and I_{R2} for the network in the Figure? (4 Marks)



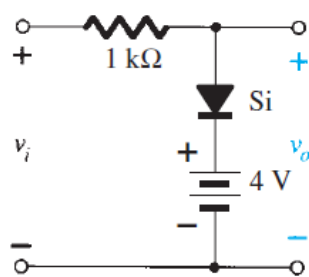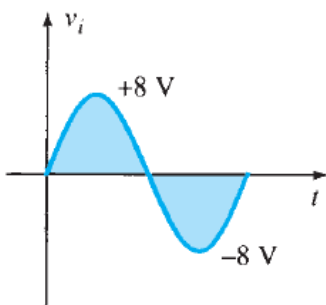2. Sketch the V_o for each network in the Figure? The diode is ideal diode (4 Marks)



(a)

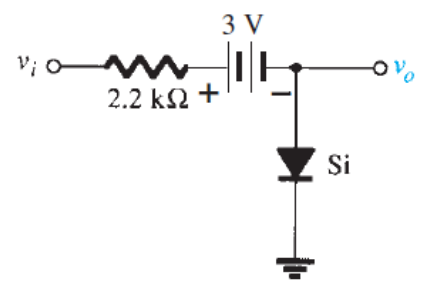

(b)

Course No: SWEN2301
Course Title: Electronics Principles
Date: 26/11/2018
No. of Questions: (4)
Time: 1 hours
Using Calculator (Yes)

University of Palestine


Second Midterm Exam
2018-2019
Total Grade:30

Instructor Name: Dr. Alaa AbuZaiter
Student No.: _____
Student Name: _____
College Name: Engineering
Dep. / Specialist: Software Eng.
Using Dictionary (No)

Question Three:

(10 Marks)

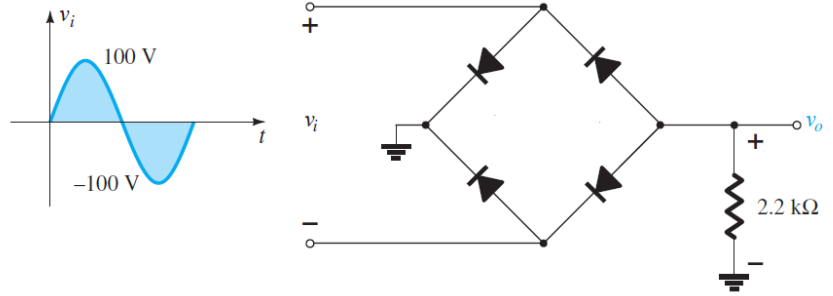1. Draw the V_o for the network of the Figure?
2. Determine the maximum current through R_L ?
3. Find the V_{DC} ?
4. If we add a capacitor to smooth the DC output voltage. Find the value of the **capacitor** (Frequency $F = 50$ Hz)?



Course No: SWEN2301
Course Title: Electronics Principles
Date: 26/11/2018
No. of Questions: (4)
Time: 1 hours
Using Calculator (Yes)

University of Palestine



Second Midterm Exam
2018-2019
Total Grade:30

Instructor Name: Dr. Alaa AbuZaiter
Student No.: _____
Student Name: _____
College Name: Engineering
Dep. / Specialist: Software Eng.
Using Dictionary (No)

Question Four:

(4 Marks)

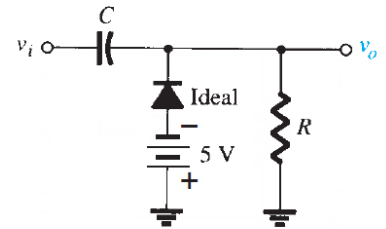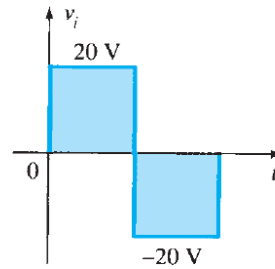1. Sketch (Draw) V_o of the network shown in the Figure. **The diode is ideal diode.**



End of Questions
Good Luck